

UNIVERSIDAD DE GUADALAJARA

CUCEI

CARRERA: INGENIERIA EN COMPUTACION

SIMULACION 9: PROGRAMACIÓN DE SISTEMAS DIGITALES EN VHDL



ALUMNO: EFRAIN ROBLES PULIDO

CODIGO: 221350095

NOMBRE DE LA MATERIA: ARQUITECTURA DE COMPUTADORAS


SECCIÓN: D10 CALENDARIO: 2021B

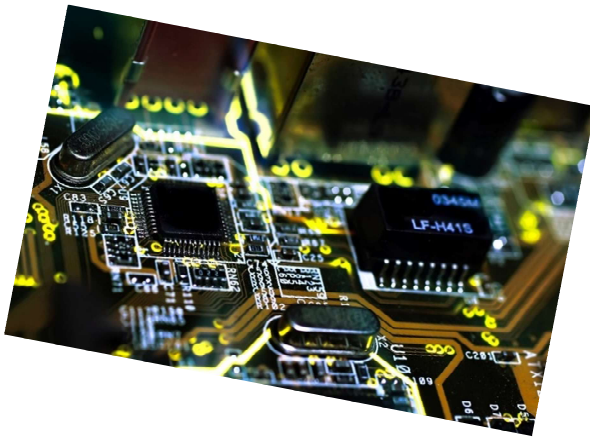 NOMBRE DE LA PROFESORA: THELMA ISABEL MORALES RAMIREZ



Simulación 9_Codigo VHDL

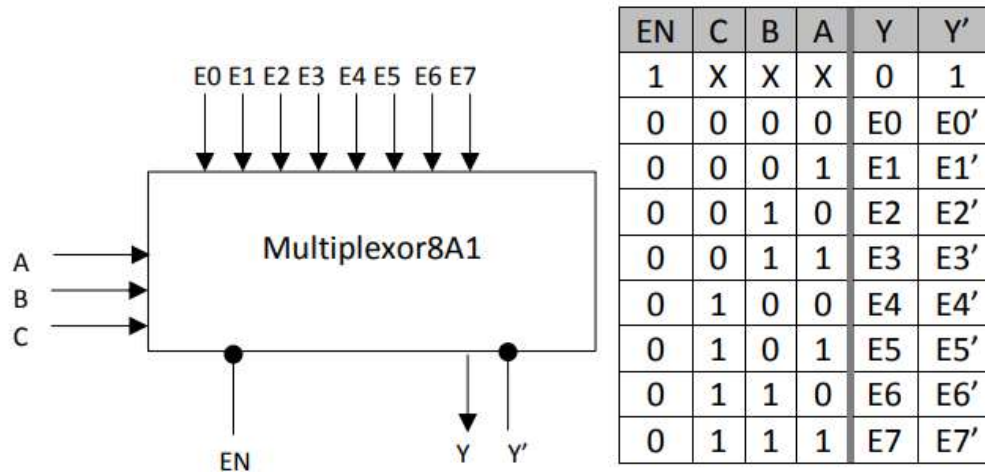- 1) Realice un programa de un multiplexor de 1 bit de salida y 8 entradas, como el que se muestra en la figura. Desarrolle su código de programación con base a la tabla de verdad.



- $Y_{not} = \sim Y$

Codigo VHDL:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Multiplexor is
    Port ( Eo : in  STD_LOGIC;--Entradas
          E1 : in  STD_LOGIC;
          E2 : in  STD_LOGIC;
          E3 : in  STD_LOGIC;
          E4 : in  STD_LOGIC;
          E5 : in  STD_LOGIC;
          E6 : in  STD_LOGIC;
          E7 : in  STD_LOGIC;

          --Selectores (A,B,C, EN)
          sel: in  STD_LOGIC_VECTOR (3 downto 0);

          --Salidas
          Y : inout STD_LOGIC;
          Ynot : out STD_LOGIC);
end Multiplexor;
```

architecture Behavioral of Multiplexor is

begin

with sel select


```
Y <= E0 when "0000",  
      E1 when "0001",  
      E2 when "0010",  
      E3 when "0011",  
      E4 when "0100",  
      E5 when "0101",  
      E6 when "0110",  
      E7 when "0111",  
      '0' when others;
```

Ynot<= not Y;


end Behavioral;

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
entity Multiplexor is  
    Port ( E0 : in  STD_LOGIC;--Entradas  
          E1 : in  STD_LOGIC;  
          E2 : in  STD_LOGIC;  
          E3 : in  STD_LOGIC;  
          E4 : in  STD_LOGIC;  
          E5 : in  STD_LOGIC;  
          E6 : in  STD_LOGIC;  
          E7 : in  STD_LOGIC;  
  
          --Selectores (A,B,C, EN)  
          sel: in  STD_LOGIC_VECTOR (3 downto 0);  
  
          --Salidas  
          Y : inout STD_LOGIC;  
          Ynot : out  STD_LOGIC);  
end Multiplexor;  
  
architecture Behavioral of Multiplexor is  
begin  
with sel select  
    Y <= E0 when "0000",  
          E1 when "0001",  
          E2 when "0010",  
          E3 when "0011",  
          E4 when "0100",  
          E5 when "0101",  
          E6 when "0110",  
          E7 when "0111",  
          '0' when others;  
  
Ynot<= not Y;  
end Behavioral;
```

Cronograma:

 

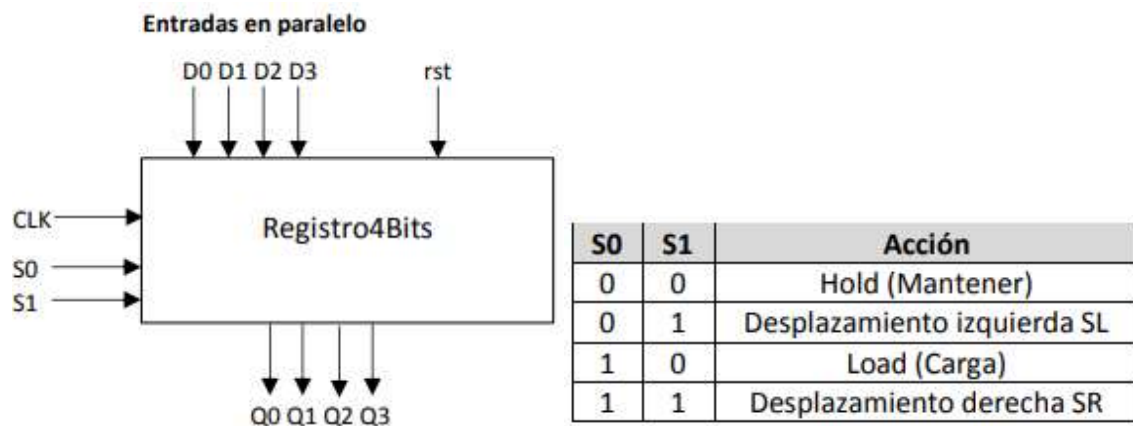- 2) Diseñe un registro de 4 bits como el mostrado en la figura, cuyo funcionamiento se encuentra regulado por las señales de control S0 y S1, tal y como se muestra en la siguiente tabla.



Codigo VHDL:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Registro is
    Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
          rst : in STD_LOGIC;
          CLK : in STD_LOGIC;
          S : in STD_LOGIC_VECTOR (1 downto 0);
          Q : inout STD_LOGIC_VECTOR (3 downto 0));
end Registro;
```

architecture Behavioral of Registro is
begin

```
process(CLK,D,S,rst)
begin
  if (rst='1') then
    Q<="0000";
  elsif (CLK' event and CLK='1') then
    if (S="00") then
      Q<=Q;
    elsif (S="01") then
      Q(3)<=Q(2);
      Q(2)<=Q(1);
      Q(1)<=Q(0);
      Q(0)<=Q(3);
    elsif (S="10") then
      Q<=D;
    elsif (S="11") then
      Q(3)<=Q(0);
      Q(2)<=Q(3);
      Q(1)<=Q(2);
      Q(0)<=Q(1);
    end if;
  end if;
end process;
```


end Behavioral;

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;


entity Registro is
  Port ( D : in  STD_LOGIC_VECTOR (3 downto 0);
        rst : in  STD_LOGIC;
        CLK : in  STD_LOGIC;
        S : in  STD_LOGIC_VECTOR (1 downto 0);
        Q : inout STD_LOGIC_VECTOR (3 downto 0));
end Registro;

architecture Behavioral of Registro is
begin
  process(CLK,D,S,rst)
  begin
    if (rst='1') then
      Q<="0000";
    elsif (CLK' event and CLK='1') then
      if (S="00") then
        Q<=Q;
      elsif (S="01") then
        Q(3)<=Q(2);
        Q(2)<=Q(1);
        Q(1)<=Q(0);
        Q(0)<=Q(3);
      elsif (S="10") then
        Q<=D;
      elsif (S="11") then
        Q(3)<=Q(0);
        Q(2)<=Q(3);
        Q(1)<=Q(2);
        Q(0)<=Q(1);
      end if;
    end if;
  end process;
end Behavioral;
```

Cronograma:

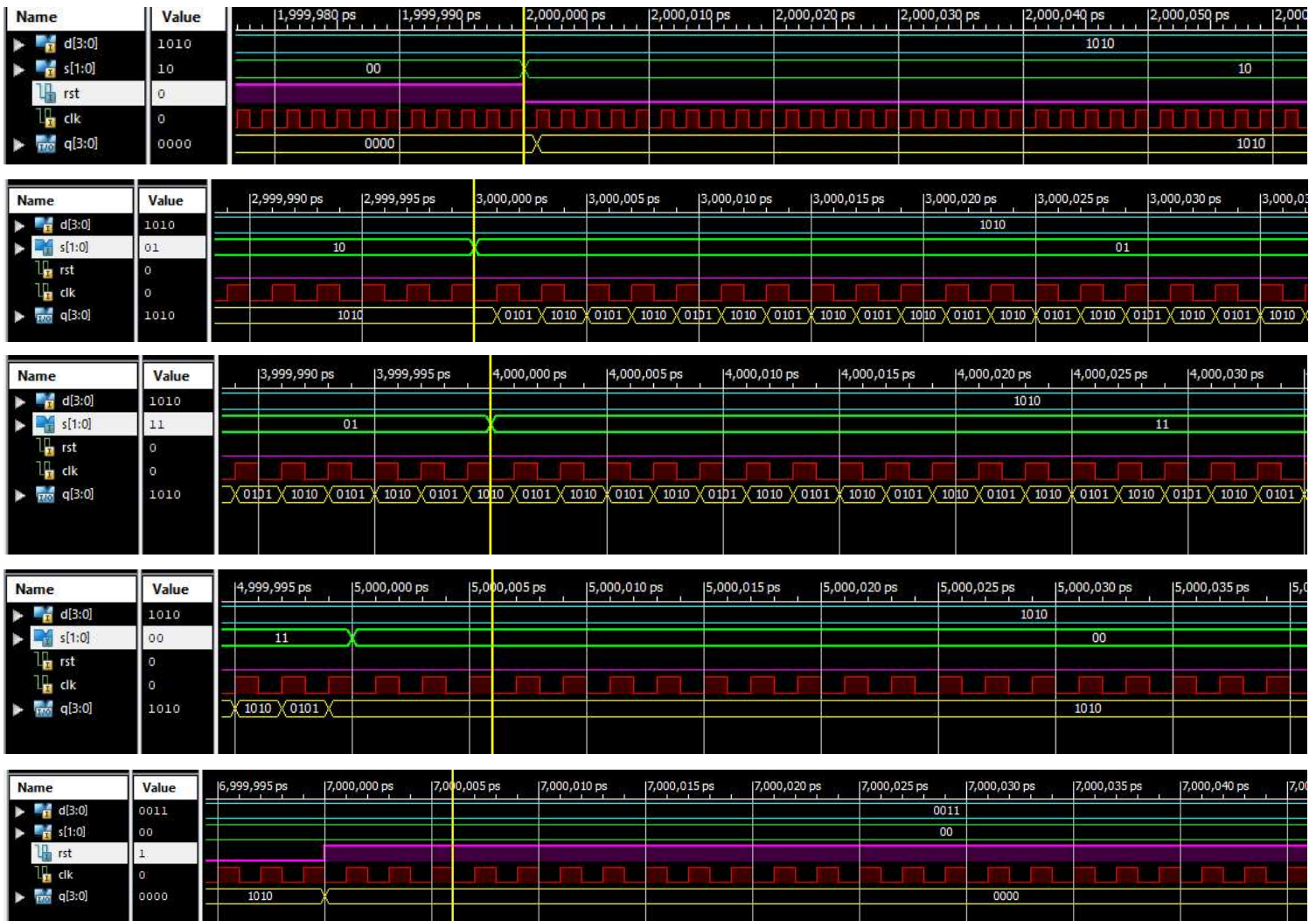

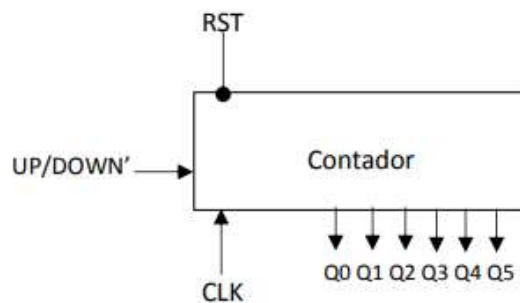- 3) Diseñe y programe un contador de 0 a 59, ascendente (1) y descendente (0). El circuito debe contar con una señal de reset activo en bajo, que coloca las salidas Q en estado bajo.



Codigo VHDL:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Contador is
  Port ( RST : in STD_LOGIC;
        U_D : in STD_LOGIC;
        CLK : in STD_LOGIC;
        Q : inout STD_LOGIC_VECTOR (5 downto 0));
end Contador;

architecture Behavioral of Contador is
begin
  process (CLK,RST,U_D)
  begin
    if(CLK'event and CLK='1') then
      if (RST='0') then
        Q<="000000";
      else
        if (U_D='1') then
          Q<=Q+1;
          if (Q="111011") then --59
            Q<="000000";--0
          end if;
        else
          Q<=Q-1;
          if (Q="000000") then --0
            Q<="111011";--59
          end if;
        end if;
      end if;
    end if;
  end process;
end Behavioral;
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Contador is
    Port ( RST : in  STD_LOGIC;
          U_D : in  STD_LOGIC;
          CLK : in  STD_LOGIC;
          Q : inout STD_LOGIC_VECTOR (5 downto 0));
end Contador;

architecture Behavioral of Contador is
begin
    process (CLK,RST,U_D)
    begin
        if (CLK'event and CLK='1') then
            if (RST='0') then
                Q<="000000";
            else
                if (U_D='1') then
                    Q<=Q+1;
                    if (Q="111011") then --59
                        Q<="000000";--0
                    end if;
                else
                    Q<=Q-1;
                    if (Q="000000") then --0
                        Q<="111011";--59
                    end if;
                end if;
            end if;
        end if;
    end process;
end Behavioral;

```


Cronograma:





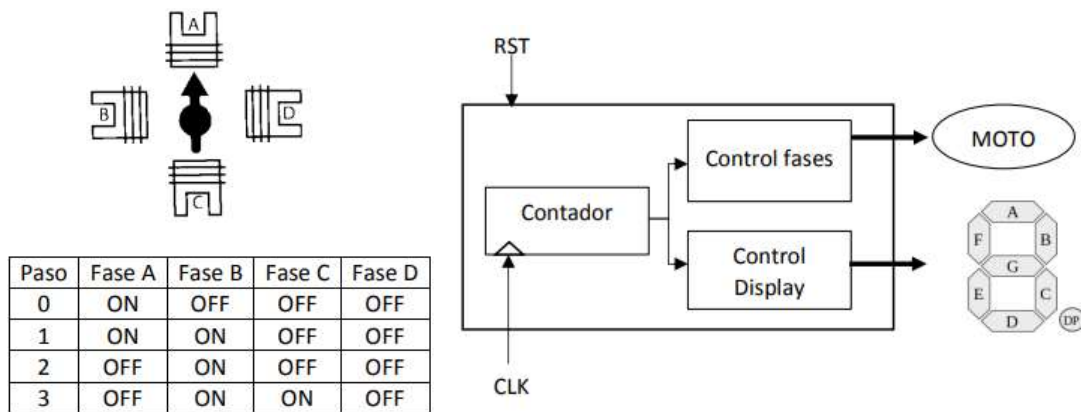4) El siguiente circuito muestra el control de encendido de un motor a pasos en secuencia de medio tiempo.

- Tiene una señal de reset que permite restablecer la secuencia de conteo inicial.
- Independiente a su control de fases, cuenta con señales de monitoreo que indican en que paso se encuentra el proceso.



Codigo VHDL:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Motor is
    Port ( RST : in STD_LOGIC;
          CLK : in STD_LOGIC;
          D : inout STD_LOGIC_VECTOR (3 downto 0);
          DIS : out STD_LOGIC_VECTOR (6 downto 0);
          Q : inout STD_LOGIC_VECTOR (1 downto 0);
          F : out STD_LOGIC_VECTOR (3 downto 0));
end Motor;
```

architecture Behavioral of Motor is
begin

```
cont: process (CLK, RST, Q)--circuito secuencial
begin
  if (RST='1') then
    Q<="00";
  elsif(CLK'event and CLK='1') then
    Q<=Q+1;
  end if;
end process cont;
```

```
deco: process (Q)--circuito combinacional
begin
  case Q is
    when "00" => D <= "1000";
    when "01" => D <= "0100";
    when "10" => D <= "0010";
    when others => D <= "0001";
  end case;
end process deco;
```

```
fase: process (D)--circuito combinacional FASES
begin
  case D is
    when "1000" => F <= "1000";
    when "0100" => F <= "1100";
    when "0010" => F <= "0100";
    when "0001" => F <= "0110";
    when others => F <= "0000";
  end case;
end process fase;
```

```
disp: process (D)--circuito combinacional DISPLAY
begin
  case D is-----abcdefg
    when "1000" => DIS <= "1111111";--8
    when "0100" => DIS <= "1001110";--12-c
    when "0010" => DIS <= "0110011";--4
    when "0001" => DIS <= "1011111";--6
    when others => DIS <= "0000000";--nada
  end case;
end process disp;
```

end Behavioral;

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Motor is
    Port ( RST : in  STD_LOGIC;
          CLK : in  STD_LOGIC;
          D : inout STD_LOGIC_VECTOR (3 downto 0);
          DIS : out  STD_LOGIC_VECTOR (6 downto 0);
          Q : inout  STD_LOGIC_VECTOR (1 downto 0);
          F : out  STD_LOGIC_VECTOR (3 downto 0));
end Motor;

architecture Behavioral of Motor is
begin
    cont: process (CLK, RST, Q)--circuito secuencial
    begin
        if (RST='1') then
            Q<="00";
        elsif (CLK'event and CLK='1') then
            Q<=Q+1;
        end if;
    end process cont;

    deco: process (Q)--circuito combinacional
    begin
        case Q is
            when "00" => D <= "1000";
            when "01" => D <= "0100";
            when "10" => D <= "0010";
            when others => D <= "0001";
        end case;
    end process deco;

```

```

    fase: process (D)--circuito combinacional FASES
    begin
        case D is
            when "1000" => F <= "1000";
            when "0100" => F <= "1100";
            when "0010" => F <= "0100";
            when "0001" => F <= "0110";
            when others => F <= "0000";
        end case;
    end process fase;

    disp: process (D)--circuito combinacional DISPLAY
    begin
        case D is-----abcdefg
            when "1000" => DIS <= "1111111";--8
            when "0100" => DIS <= "1001110";--12-c
            when "0010" => DIS <= "0110011";--4
            when "0001" => DIS <= "1011111";--6
            when others => DIS <= "0000000";--nada
        end case;
    end process disp;
end Behavioral;

```

Cronograma:

